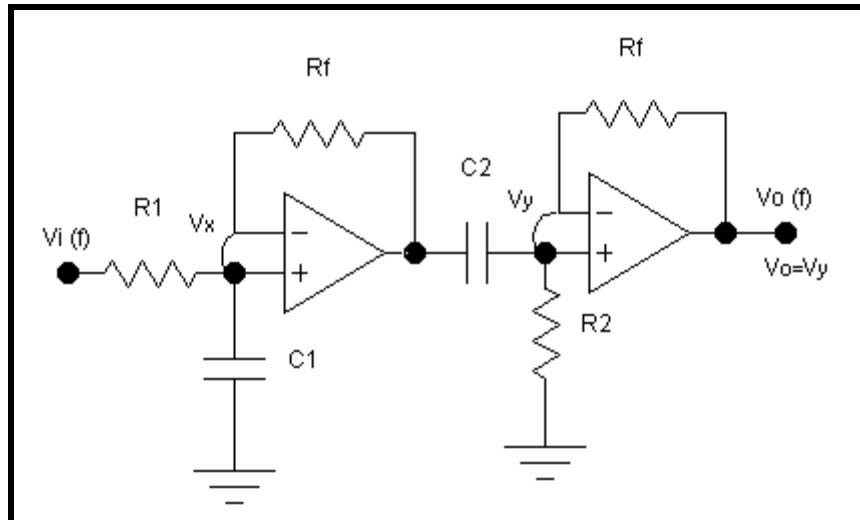


FILTRO PASABANDA: BANDA ANCHA



a. Hallar  $A_v(w) = f(R, C, w)$

$$V_x = \frac{Z_{c1}}{R_1 + Z_{c1}} V_i \rightarrow V_x = \frac{1}{R_1 + \frac{1}{jwC}} V_i \rightarrow V_x = \frac{1}{jwR_1C_1 + 1} V_i \quad (1)$$

$$V_y = \frac{R_2}{R_2 + Z_{c2}} V_x \rightarrow V_o = \frac{R_2}{R_2 + \frac{1}{jwC_2}} V_x \rightarrow V_o = \frac{jwR_2C_2}{jwR_2C_2 + 1} V_x \quad (2)$$

Reemplazo 1 en 2

$$V_o = \frac{jwR_2C_2}{jwR_2C_2 + 1} \left[ \frac{1}{jwR_1C_1 + 1} V_i \right] \rightarrow V_o = \frac{jwR_2C_2}{(jwR_2C_2 + 1)(jwR_1C_1 + 1)} V_i$$

$$\frac{V_o}{V_i} = \frac{jwR_2C_2}{-w^2R_1R_2C_1C_2 + jwR_2C_2 + jwR_1C_1 + 1}$$

$$|A_v(w)| = \frac{wR_2C_2}{\sqrt{(1 - w^2R_1R_2C_1C_2)^2 + (wR_2C_2 + wR_1C_1)^2}}$$

b. Hallar  $w_c$  y  $f_c$



$$\frac{1}{\sqrt{2}} = \frac{wR_2C_2}{\sqrt{(1-w^2R_1R_2C_1C_2)^2 + (wR_2C_2 + wR_1C_1)^2}}$$

$$\left( \sqrt{(1-w^2R_1R_2C_1C_2)^2 + (wR_2C_2 + wR_1C_1)^2} \right)^2 = (wR_2C_2\sqrt{2})^2$$

$$(1-w^2R_1R_2C_1C_2)^2 + (wR_2C_2 + wR_1C_1)^2 = 2w^2R_2^2C_2^2$$

$$1 - 2w^2R_1R_2C_1C_2 + w^4R_1^2R_2^2C_1^2C_2^2 + w^2R_2^2C_2^2 + 2w^2R_1R_2C_1C_2 + w^2R_1^2C_1^2 = 2w^2R_2^2C_2^2$$

$$1 + w^4R_1^2R_2^2C_1^2C_2^2 - w^2R_2^2C_2^2 + w^2R_1^2C_1^2 = 0$$

Como:  $f_H = 10f_L$ , entonces:

$$f_L = \frac{1}{2\pi R_2C_2} \quad f_H = \frac{10}{2\pi R_2C_2} = \frac{1}{2\pi R_1C_1} \quad R_2C_2 = 10R_1C_1$$

Lo reemplazo en la ecuación anterior:

$$1 + w^4R_1^2C_1^2(10R_2C_2)^2 - w^2(10R_1C_1)^2 + w^2R_1^2C_1^2 = 0$$

$$1 + 100w^4R_1^4C_1^4 - 100w^2R_1^2C_1^2 + w^2R_1^2C_1^2 = 0$$

$$100w^4R_1^4C_1^4 - 99w^2R_1^2C_1^2 + 1 = 0$$

$$w^2(100w^2R_1^4C_1^4 - 99R_1^2C_1^2) + 1 = 0$$

$$w^2 + 1 = 0$$

$$100w^2R_1^4C_1^4 - 99R_1^2C_1^2 = 0$$

$$w = \sqrt{-1}$$

$$w^2 = \frac{99R_1^2C_1^2}{100R_1^4C_1^4} \rightarrow w = \sqrt{\frac{99}{100R_1^2C_1^2}} \rightarrow \boxed{w = \frac{\sqrt{99}}{10R_1C_1}}$$

$$2\pi f_H = \frac{\sqrt{99}}{10R_1C_1} \rightarrow f_H = \frac{\sqrt{99}}{20\pi R_1C_1} \rightarrow \boxed{f_H = \frac{0.1583}{R_1C_1}} \rightarrow$$

$$f_L = \frac{0.1583}{10R_1C_1}$$

$$\boxed{f_L = \frac{0.01583}{R_1C_1}}$$

c. Hallar  $|A_v(f)| = f(f, f_c)$



$$f_r = \sqrt{\left(\frac{0.1583}{R_1 C_1}\right)\left(\frac{0.01583}{R_1 C_1}\right)} = \frac{0.05}{R_1 C_1} \rightarrow \boxed{R_1 C_1 = \frac{0.05}{f_r}}$$

$$|A_v(\omega)| = \frac{10\omega\left(\frac{0.05}{f_r}\right)}{\sqrt{\left(1-10\omega^2\left(\frac{0.05}{f_r}\right)^2\right)^2 + \left(11\omega\left(\frac{0.05}{f_r}\right)\right)^2}}$$

$$\boxed{|A_v(\omega)| = \frac{3.1415\left(\frac{f}{f_r}\right)}{\sqrt{\left(1-0.986\left(\frac{f}{f_r}\right)^2\right)^2 + \left(3.4557\left(\frac{f}{f_r}\right)\right)^2}}}$$

d. Dibujar  $|A_v(f)|$  Vs  $f$

$$\boxed{|A_v(\omega)| = \frac{3.1415\left(\frac{f}{f_r}\right)}{\sqrt{\left(1-0.986\left(\frac{f}{f_r}\right)^2\right)^2 + \left(3.4557\left(\frac{f}{f_r}\right)\right)^2}}}$$

$$\boxed{A_v = 20 \log \left( \frac{V_o}{V_i} \right)}$$

f	$ A_v(f) $	$ A_v(f) $ db
0	0	0
0.1 fc	0.3	-10
0.5 fc	0.8	-2
0.8 fc	0.9	-1
fc	0.9	-1
2 fc	0.8	-2
4 fc	0.6	-4
6 fc	0.5	-7
8 fc	0.4	-9
10 fc	0.3	-10